Q

999 Likes

PMOLED display Manufacturer

0.49"-5.5" PMOLED display

WINSTAR Display offers competitive price and high quality PMOLED display.

winstar.com.tw


OPEN

TIP122 - Darlington NPN Transistor

18 December 2017 - 0 Comments



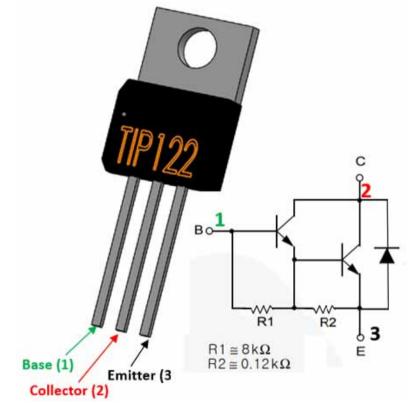(/sites/default/files/components/TIP122-transistor.jpg)



(/sites/default/files/component_pin/TIP122-Darlington-NPN-Transistor.jpg)

TIP122 Transistor Pinout

TIP122 Transistor



Pin Configuration:

Pin Number	Pin Name	Description
1	Base	Controls the biasing of transistor, Used to turn ON or OFF the transistor
2	Collector	Current flows in through collector, normally connected to load
3	Emitter	Current Drains out through emitter, normally connected to ground

Features:

Darlington Medium-power NPN Transistor

101 (/

Q

- Collector-Base voltage (VCB) is 100V
- Emitter Base Voltage (VBE) is 5V
- Base Current(IB) is 120mA
- Available in To-220 Package

99 te: Complete Technical Details can be found at the **TIP122 datasheet** given at the end of this page. Likes

Alternative NPN Transistors:

C549, BC636, BC639, BC547 (https://components101.com/bc547-transistor-pinout-datasheet), 2N2369, 2N3055, 2N3904 (https://components101.com/2n3904-pinout-datasheet), 2N3906 (https://components101.com/2n3906-pinout-equivalent-datasheet), 2SC5200



TIP122 Equivalent Transistors:


TIP127 (PNP), 2N6045, 2N6532, 2SD1415, 2SD2495, BDT63, BDW2, KSB601, KSD560, MJF6388

Same Family Transistors:

TIP120, TIP121, TIP122 (NPN); TIP125, TIP126, TIP127 (PNP)

About TIP122:

The **TIP122** is a Darlington pair NPN transistor. It functions like a normal NPN transistor, but since it has a Darlington pair inside it has a good collector current rating of about 5A and a gain of about 1000. It can also withstand about 100V across its collector- Emitter hence can be used to drive heavy loads. The Darlington pair inside this transistor is shown clearly as its internal circuit schematic below

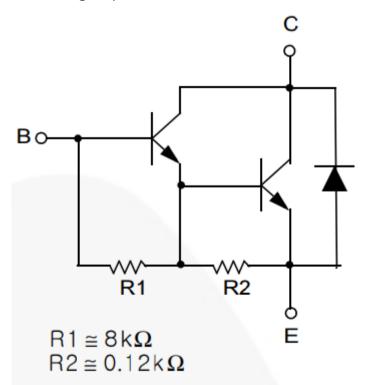

As you can see, there are two transistors inside this TO-220 package in which the emitter of the first transistor is connected with the base of the second transistor and the collector of both transistors are connected together to form a Darlington pair. This increases the current gain and current rating of this transistor.

Where to TIP122:


101 (/)

Q

So, if you looking for a transistor that could be easily controlled by a Logic device to switch high power loads or to amplify high current then this Transistor might be an ideal choice for your application.

How to use TIP122:

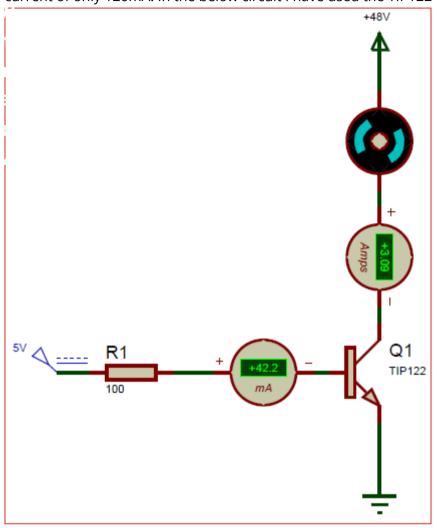999though TIP has high collector current and current gain, it is fairly simple to control the device since it has an Emitter-Base voltage (VBE) of only 5V and base current of only 120mA. In the below circuit I have used the TIP122 to control a 48V motor which has a continuous current of about 3A.



The continues collector current of this transistor is 5A and our load consumes only 3A which is fine. The maximum base current is about 120mA, but I have used high value of 100ohm resistor to limit it to 42mA. You can use even a 1K resistor if your collector current requirement is less. The peak (pulse) current of this transistor is 8A so make sure your motor does not consume more than that. This is just a model circuit diagram that shows the working on this transistor it cannot be used as such. So, similarly you can control your load in the same way.


Applications


- Can be used to switch high current (upto 5A) loads
- Can be used as medium Power switches
- Used where high amplification is needed
- Speed control of Motors
- Inverter and other rectifier circuits

2D-Model

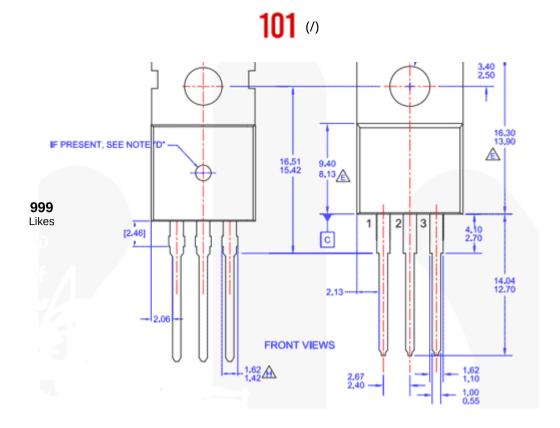2D dimensions will help you in placing this component at the time of making circuit on perf board or a PCB.





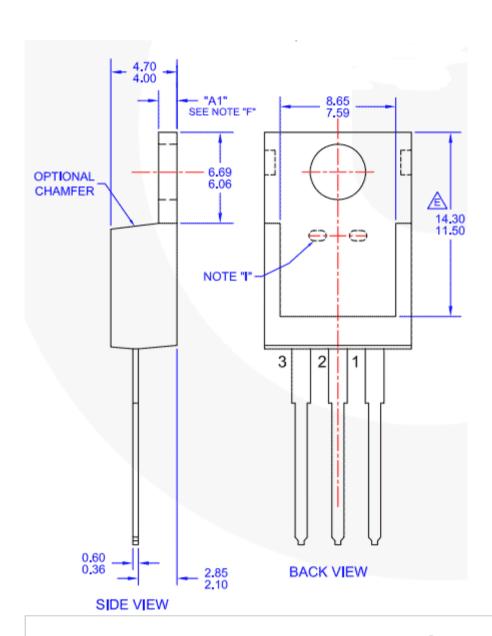

Component Datasheet TIP122 Transistor Datasheet

(https://components101.com/sites/default/files/component_datasheet/TIP122%20-%20Darlington%20NPN%20Transistor.pdf)

Tags

NPN TRANSISTOR (/TAGS/NPN-TRANSISTOR)

TRXF (thermal protected)

999 Likes setfuse.com

2N2222A Pinout, Features, Equivalent manufacturer & Datasheet

Leading encoder

2N3904 Transistor Pinout, Equivalent, Features &...

components101.com

Ad RLS

components101.con

Microwave Amplifiers

Ad ampsa.com

TIP31C Transistor Pinout, Configuration,

Equivalent, Circuit...

components101.com

BC549 NPN Transistor Pinout, Features,...

components101.com

S8550 Trans Pinout, Data Features &.

components101.con

101 (/)

Q

999 Likes



999 Likes









(/articles/relays-and-contactor-types-working-and-difference-between-them-0)

Relays and Contactors: Types, Working and Difference between them (/articles/relays-and101 (/)





101

Components101 is a resource dedicated for electronics design engineers, covering product news, analysis and articles on latest electronics components.

IMPORTANT LINKS

- > Contact
- > Advertise
- > Privacy Policy
- > Cookie Policy

POPULAR TAGS

Power Electronics (/tags/power-electronics)

NPN Transistor (/tags/npn-transistor)

Embedded (/tags/embedded)

Automotive (/tags/automotive)

PNP Transistor (/tags/pnp-transistor)

voltage regulator (/tags/voltage-regulator)

https://components 101.com/tip122-pinout-equivalent-data sheet

101 (/) email address

Q

Subscribe

999 Likes Copyright 2019 © Components101. All rights reserved